
AVR1012: XMEGA A Schematic Checklist

Features

- Power Supplies
- Backup battery for XMEGA A3B
- Reset circuit
- Clocks and crystal oscillators
- External bus interface
- JTAG and PDI

1 Introduction

A good hardware design comes from a proper schematic. Since XMEGA™ A devices have a fair number of pins and functions, the schematic for these devices can be large and quite complex.

This application note describes a common checklist which should be used when starting and reviewing the schematics for a XMEGA A design.



8-bit **AVR**®
Microcontrollers

Application Note

Rev. 8278A-AVR-12/09



2 Power Supplies

2.1 Power Supply Connections

Figure 2-1. Power Supply schematic

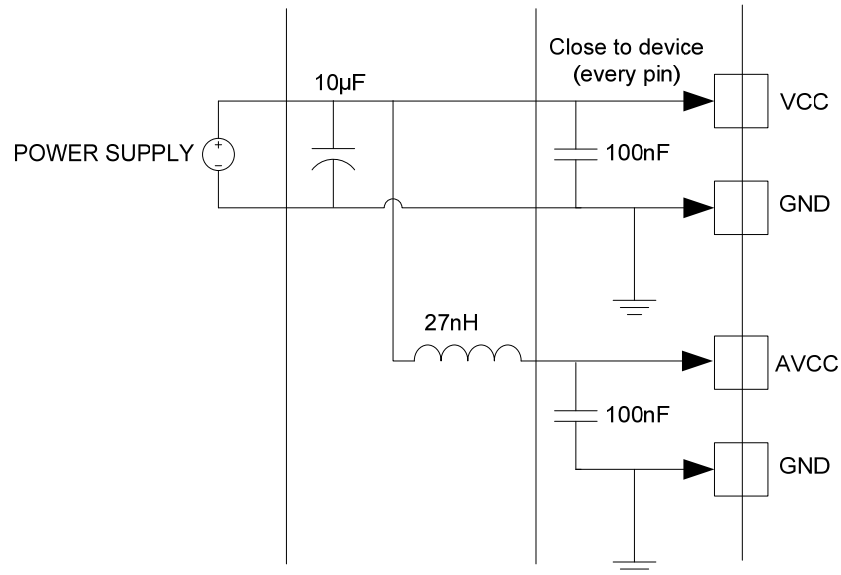


Table 2-1. Power Supply Connections

Signal name	Recommended pin connection	Description
VCC	1.6 V to 3.6 V Decoupling/filtering capacitors 100 nF ⁽¹⁾⁽²⁾ and 10 µF ⁽¹⁾	Digital supply voltage
AVCC	1.6 V to 3.6 V Decoupling/filtering capacitors 100 nF ⁽¹⁾⁽²⁾ and 10 µF ⁽¹⁾ Inductor improves power filtering 27nH ⁽¹⁾⁽³⁾	Analog supply voltage
GND		Ground

1. These values are given only as a typical example.

2. Decoupling capacitor should be placed close to the device for each supply pin pair in the signal group, low ESR caps should be used for better decoupling.

3. The Inductor value is decided by the formula as below $f_{cut} = \frac{1}{2\pi\sqrt{LC}}$

Notes

Assume cut-off frequency $f_{cut} = 3.2MHz$ and $C = 100nF$, so get $L = 27nH$

2.2 Battery Backup Module Connections

This section is only for the application which uses the battery backup function of the XMEGA A3B devices, such as the ATxmega256A3B. Upon main power loss the device will detect this and automatically switch the Battery Backup Module to be powered from the VBAT pin.

Figure 2-2. Battery Backup Module Schematic

 


Table 2-2. Battery Backup Module Connections

Signal name	Recommended pin connection	Description
VBAT	1.8 V to 3.6 V	Battery Backup Module supply voltage
GND		Ground

Notes To run the Real Time Counter a 32.768 kHz crystal oscillator must be connected between the TOSC1 and TOSC2 pins when running from VBAT.

2.3 External Analog Reference Connections

The following schematic checklist is only necessary if the design is using the external analog reference. If the internal reference is used, the circuit is not necessary.

Figure 2-3. External Analog Reference schematic with Two References

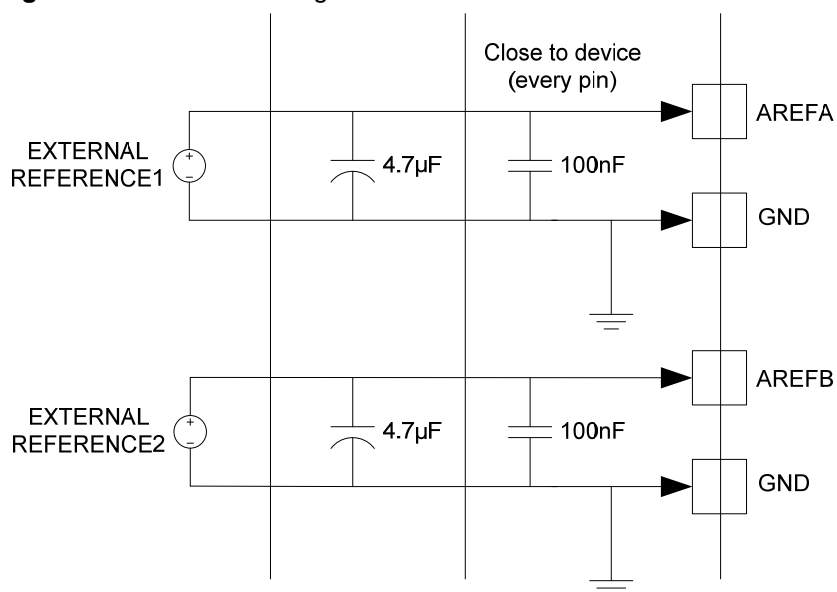


Figure 2-4. External Analog Reference schematic with One Reference

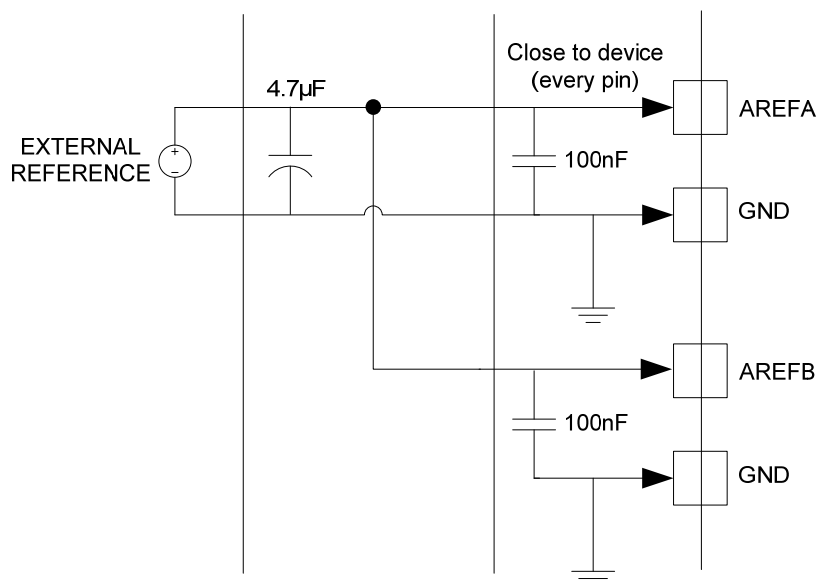


Table 2-3. External Analog Reference Connections

Signal name	Recommended pin connection	Description
AREFA	1.0V to AVCC-0.6V for ADC 1.1V to AVCC-0.6V for DAC Decoupling/filtering capacitors 100 nF ⁽¹⁾⁽²⁾ and 4.7 μF ⁽¹⁾	External reference from AREF pin on PORT A.
AREFB	1.0V to AVCC-0.6V for ADC 1.1V to AVCC-0.6V for DAC Decoupling/filtering capacitors 100 nF ⁽¹⁾⁽²⁾ and 4.7 μF ⁽¹⁾	External reference from AREF pin on PORT B.
GND		Ground

- Notes
1. These values are given only as a typical example.
 2. Decoupling capacitor should be placed close to the device for each supply pin pair in the signal group.



3 External Reset circuit

The external reset circuit is connected to RESET pin when the external reset function is used. If internal reset is used, the circuit is not necessary. The reset switch also can be removed, if the manual reset is not necessary.

Figure 3-1. External Reset circuit example schematic

 


Table 3-1. Reset circuit Connections

Signal name	Recommended pin connection	Description
RESET	Reset low level threshold voltage VCC = 2.7 - 3.6V: Below 0.45*VCC VCC = 1.6 - 2.7V: Below 0.42*VCC	Reset pin

This pull-up resistor makes sure that reset does not go low unintended. When the PDI programming and debugging is used, the reset line is used as clock. The reset pull-up should be 10k or weaker, or be removed altogether.

Notes Any reset capacitors should be removed if PDI programming and debugging is used. Other external reset sources should be disconnected.

4 Clocks and crystal oscillators

4.1 External clock source

Figure 4-1. External clock source example schematic

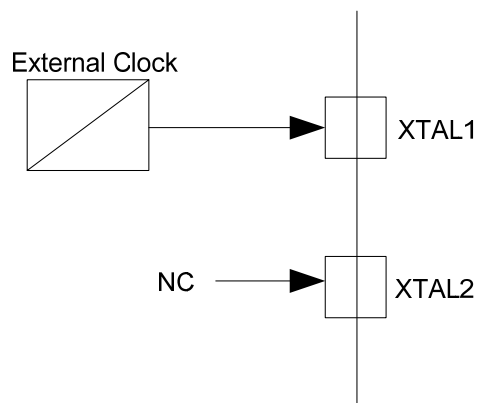


Table 4-1. External clock source Connections

Signal name	Recommended pin connection	Description
XTAL1	XTAL1 is used as input for an external clock signal	Input for inverting Oscillator pin 1
XTAL2	Can be left unconnected or used as GPIO	

4.2 Crystal oscillator

Figure 4-2. Crystal oscillator example schematic

 


Table 4-2. Crystal oscillator checklist

Signal name	Recommended pin connection	Description
XTAL1	Biasing capacitor 15 pF ⁽¹⁾⁽²⁾	External crystal between 0.4 MHz to 16 MHz
XTAL2	Biasing capacitor 15 pF ⁽¹⁾⁽²⁾	

1. These values are given only as a typical example. Please refer to the crystal datasheet to determine the capacitor value for the crystal used or refer to the application note “AVR1003: Using the XMEGA Clock System”.

Notes 2. Decoupling capacitor should be placed close to the device for each supply pin pair in the signal group.

4.3 External Real Time Oscillator

The Low-frequency Crystal Oscillator is optimized for use with a 32.768 kHz watch crystal. When selecting crystals, load capacitance and crystal's Equivalent Series Resistance, ESR must be taken into consideration. Both values are specified by the crystal vendor.

XMEGA oscillator is optimized for very low power consumption, and thus when selecting crystals, see Table 4-3 for maximum ESR recommendations on 9 pF and 12.5 pF crystals.


The Low-frequency Crystal Oscillator provides an internal load capacitance of typical 8.0 pF. Crystals with recommended 8.0 pF load capacitance can be without external capacitors as shown in Figure 4-3.

Table 4-3. Maximum ESR Recommendation for 32.768 kHz Watch Crystal

Crystal CL (pF)	Max ESR [kΩ] ⁽¹⁾
9.0	65
12.5	30

Note: 1. Maximum ESR is typical value based on characterization

Figure 4-3. External real time oscillator without biasing capacitor

 

Crystals specifying load capacitance (CL) higher than 8.0 pF, require external capacitors applied as described in Figure 4-4.

To find suitable load capacitance for a 32.768 kHz crystal, please consult the crystal datasheet.

Figure 4-4. External real time oscillator with biasing capacitor

 


Table 4-4. External real time oscillator checklist

Signal name	Recommended pin connection	Description
TOSC1	Biasing capacitor 22 pF ⁽¹⁾⁽²⁾	Timer Oscillator pin 1
TOSC2	Biasing capacitor 22 pF ⁽¹⁾⁽²⁾	Timer Oscillator pin 2

1. These values are given only as a typical example. Please refer to the crystal datasheet to determine the capacitor value for the crystal used or refer to the application note "AVR1003: Using the XMEGA Clock System".

Notes 2. Decoupling capacitor should be placed close to the device for each supply pin pair in the signal group.

5 External bus interface


The External Bus Interface (EBI) is the interface for connecting external peripheral and memory to access it through the data memory space.

The EBI can interface external SRAM, SDRAM, and/or peripherals such as LCD displays and other memory mapped devices.

5.1 SRAM Configuration


5.1.1 8-bit SRAM No Multiplexing

Figure 5-1. 8-bit SRAM No Multiplexing Connection

 


5.1.2 8-bit SRAM Multiplexing Address Byte 0 and 1

Figure 5-2. 8-bit SRAM Multiplexing address byte 0 and 1 Connection

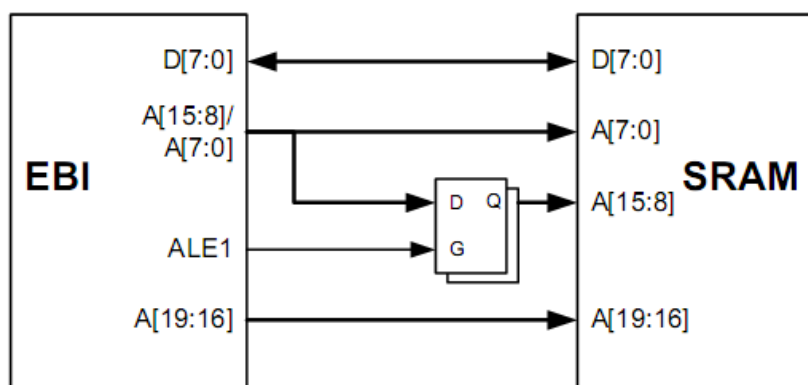


5.1.3 8-bit SRAM Multiplexing Address Byte 0 and 2

Figure 5-3. 8-bit SRAM Multiplexing address byte 0 and 2 Connection

 

5.1.4 8-bit SRAM Multiplexing Address Byte 0, 1 and 2


Figure 5-4. 8-bit SRAM Multiplexing address byte 0 ,1 and 2 Connection

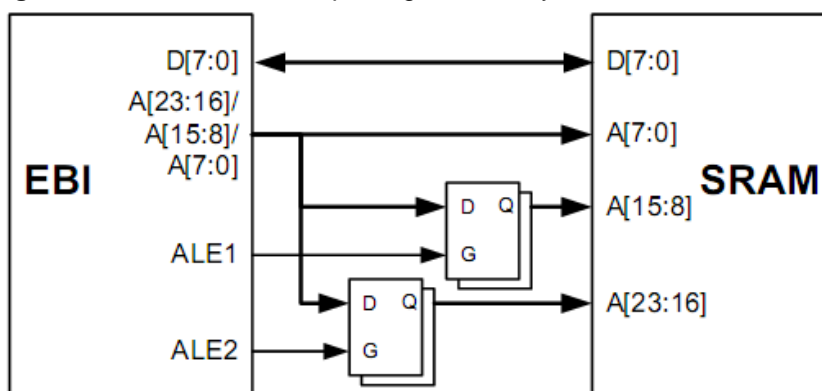

5.2 The SRAM Low Pin Count (LPC) configuration


5.2.1 8-bit SRAM Multiplexing Data with Address Byte 0

Figure 5-5. 8-bit SRAM Multiplexing Data with Address Byte 0 Connection

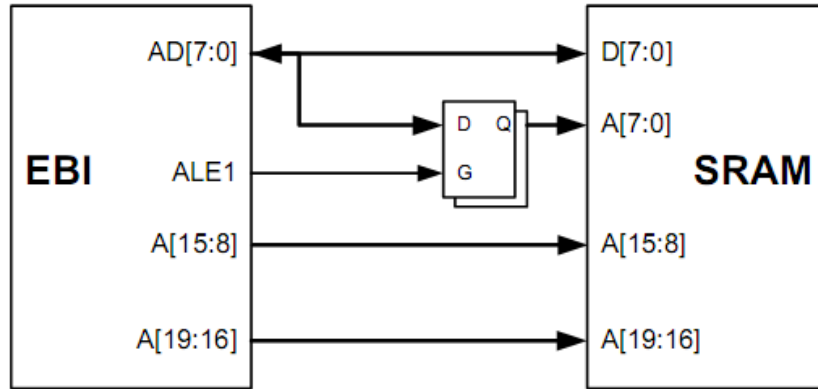

5.2.2 8-bit SRAM Multiplexing Data with Address Byte 0 and 1


Figure 5-6. 8-bit SRAM Multiplexing Data with Address Byte 0 and 1 Connection

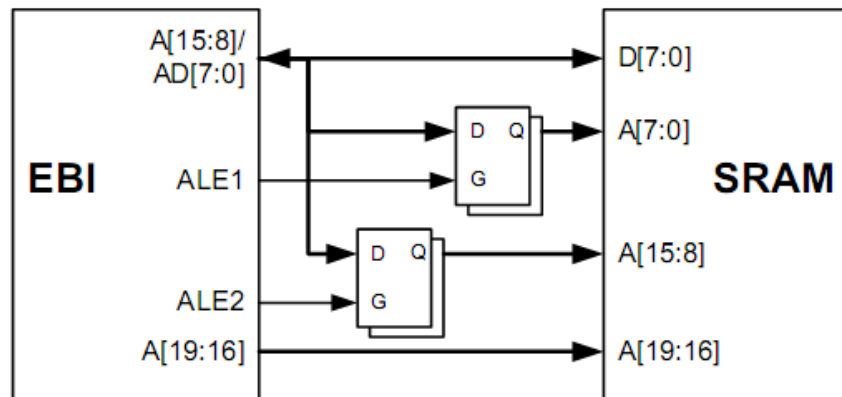

5.3 SDRAM Configuration

5.3.1 4-bit SDRAM 3-Port EBI Configuration

Figure 5-7. 4-bit SDRAM 3-Port EBI Configuration

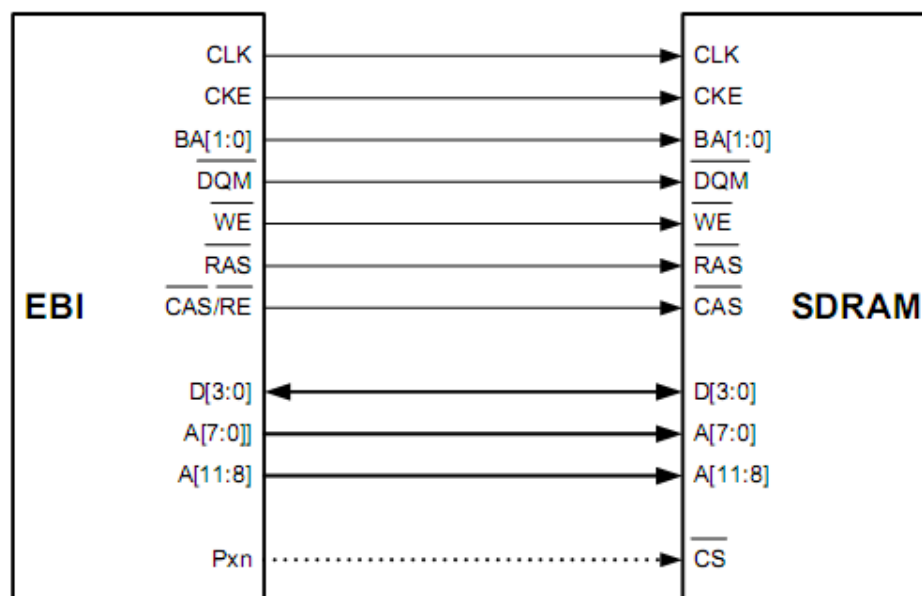

6 JTAG and PDI ports

6.1 JTAG port interface

Figure 6-1. JTAG port interface example schematic

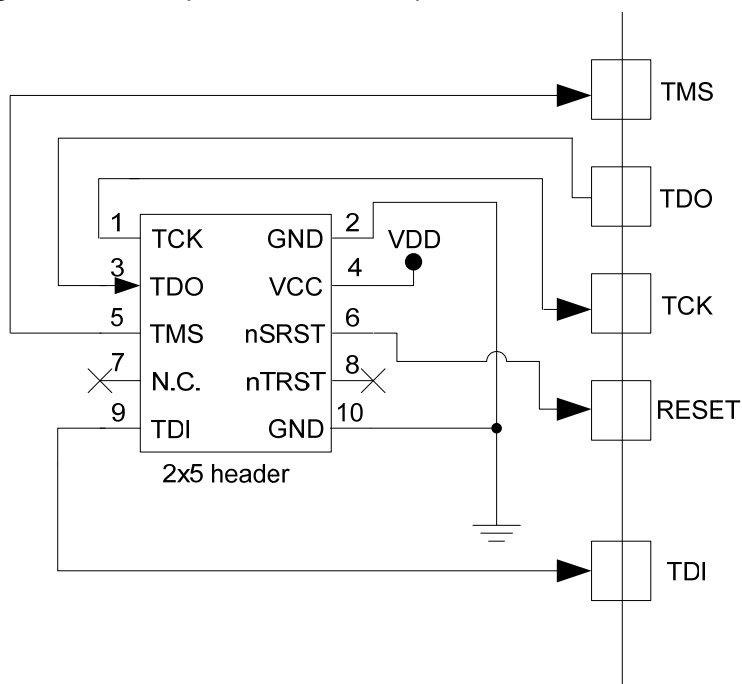


Table 6-1. JTAG port interface checklist

Signal name	Description
TMS	Test mode select, sampled on rising TCK.
TDO	Test data output, driven on falling TCK.
TCK	Test clock, fully asynchronous to system clock frequency.
RESET	Device external reset line.
TDI	Test data input, sampled on rising TCK.

6.2 PDI port interface

Figure 6-2. PDI port interface example schematic

 


Table 6-2. PDI port interface checklist

Signal name	Recommended pin connection	Description
PDI_CLK	This pull-up resistor makes sure that reset does not go low unintended. When the PDI programming and debugging is used, the reset line is used as clock. The reset pull-up should be 10k or weaker, or be removed altogether. Any reset capacitors should be removed if PDI programming and debugging is used. Other external reset sources should be disconnected.	PDI clock input / Reset pin
PDI_DATA		PDI_DATA: PDI data input/output



7 Suggested reading

7.1 Device datasheet

The device datasheet contains block diagrams of the peripherals and details about implementing firmware for the device. The datasheet is available on <http://www.atmel.com/AVR> in the Datasheets section.

7.2 Evaluation kit schematic

The evaluation kit ATAVRXPLAIN contains the full schematic for the board; it can be used as a reference design. The schematic is available on <http://www.atmel.com/AVR> in the Tools & Software section.



Headquarters

Atmel Corporation
2325 Orchard Parkway
San Jose, CA 95131
USA
Tel: 1(408) 441-0311
Fax: 1(408) 487-2600

International

Atmel Asia
Unit 1-5 & 16, 19/F
BEA Tower, Millennium City 5
418 Kwun Tong Road
Kwun Tong, Kowloon
Hong Kong
Tel: (852) 2245-6100
Fax: (852) 2722-1369

Atmel Europe
Le Krebs
8, Rue Jean-Pierre Timbaud
BP 309
78054 Saint-Quentin-en-
Yvelines Cedex
France
Tel: (33) 1-30-60-70-00
Fax: (33) 1-30-60-71-11

Atmel Japan
9F, Tonetsu Shinkawa Bldg.
1-24-8 Shinkawa
Chuo-ku, Tokyo 104-0033
Japan
Tel: (81) 3-3523-3551
Fax: (81) 3-3523-7581

Product Contact

Web Site
<http://www.atmel.com/>

Technical Support
avr@atmel.com

Sales Contact
www.atmel.com/contacts

Literature Request
www.atmel.com/literature

Disclaimer: The information in this document is provided in connection with Atmel products. No license, express or implied, by estoppel or otherwise, to any intellectual property right is granted by this document or in connection with the sale of Atmel products. **EXCEPT AS SET FORTH IN ATMEL'S TERMS AND CONDITIONS OF SALE LOCATED ON ATMEL'S WEB SITE, ATMEL ASSUMES NO LIABILITY WHATSOEVER AND DISCLAIMS ANY EXPRESS, IMPLIED OR STATUTORY WARRANTY RELATING TO ITS PRODUCTS INCLUDING, BUT NOT LIMITED TO, THE IMPLIED WARRANTY OF MERCHANTABILITY, FITNESS FOR A PARTICULAR PURPOSE, OR NON-INFRINGEMENT. IN NO EVENT SHALL ATMEL BE LIABLE FOR ANY DIRECT, INDIRECT, CONSEQUENTIAL, PUNITIVE, SPECIAL OR INCIDENTAL DAMAGES (INCLUDING, WITHOUT LIMITATION, DAMAGES FOR LOSS OF PROFITS, BUSINESS INTERRUPTION, OR LOSS OF INFORMATION) ARISING OUT OF THE USE OR INABILITY TO USE THIS DOCUMENT, EVEN IF ATMEL HAS BEEN ADVISED OF THE POSSIBILITY OF SUCH DAMAGES.** Atmel makes no representations or warranties with respect to the accuracy or completeness of the contents of this document and reserves the right to make changes to specifications and product descriptions at any time without notice. Atmel does not make any commitment to update the information contained herein. Unless specifically provided otherwise, Atmel products are not suitable for, and shall not be used in, automotive applications. Atmel's products are not intended, authorized, or warranted for use as components in applications intended to support or sustain life.

© 2009 Atmel Corporation. All rights reserved. Atmel®, Atmel logo and combinations thereof, AVR®, AVR® logo and others, are the registered trademarks, XMEGA™ and others are trademarks of Atmel Corporation or its subsidiaries. Other terms and product names may be trademarks of others.